



DEEC

DEPARTAMENTO DE ENGENHARIA
ELETROTÉCNICA E DE COMPUTADORES

TÉCNICO LISBOA

Arquitectura de Computadores ***MEEC (2016/17 – 2º Sem.)***

Utilização do VIVADO

Prof. Nuno Horta

UNIDADE DE PROCESSAMENTO

Projeto no VIVADO (Abrir Projecto)

The screenshot displays the Vivado 2016.4 interface. The 'Quick Start' panel on the left has the 'Open Project' button circled in red. The 'Open Project' dialog box is open, showing the project files, with 'projeto.sim' circled in red. The 'Project Manager' window shows the project structure, with 'DataPath - structural (DataPath.vhd) (3)' circled in red. The 'Project Summary' window shows project settings, and the 'Design Runs' table is visible at the bottom.

Project Summary

Project Settings

Project name: projeto
Project location: C:/Users/NHorta/Desktop/ACOMP 20162017 aulas/projeto/projeto
Product family: Artix-7
Project part: xc7a35tfgq256-1
Top module name: DataPath
Target language: VHDL
Simulator language: Mixed

Synthesis

Status: Not started
Messages: No errors or warnings

Implementation

Status: Not started
Messages: No errors or warnings

Design Runs

Name	Constraints	Status	WNS	TNS	WHS	THS	TPWS	Total Power	Failed Routes	LUT	FF	BRAM	URAM	PCle %	Start
synth_1	constrs_1	Not started													
impl_1	constrs_1	Not started													

VHDL – Lab1

DATAPATH

REGISTER

FUNCTIONALUNIT

DATAMEMORY

```
DataPath.vhd
C:/Users/IT-ICGLX-ADMIN/Desktop/DP/project_2014.2/srcs/sources_1/imports/sources_1/new/DataPath.vhd

1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3
4 entity DataPath is
5     Port (
6         AA : in std_logic_vector (3 downto 0);
7         BA : in std_logic_vector (3 downto 0);
8         DA : in std_logic_vector (3 downto 0);
9         WR : in std_logic;
10        MA : in std_logic;
11        MB : in std_logic;
12        KNS : in std_logic_vector (15 downto 0);
13        CLK : in std_logic;
14        MW : in std_logic;
15        FS : in std_logic_vector (3 downto 0);
16        MD : in std_logic;
17        D : out std_logic_vector (15 downto 0);
18        FL : out std_logic_vector (3 downto 0));
19 end DataPath;
20
21 architecture structural of DataPath is
22     component RegisterFile is
23         Port ( CLK : in std_logic;
24             Data : in std_logic_vector (15 downto 0);
25             WR : in std_logic;
26             DA : in std_logic_vector (3 downto 0);
27             AA : in std_logic_vector (3 downto 0);
28             BA : in std_logic_vector (3 downto 0);
29             A : out std_logic_vector (15 downto 0);
30             B : out std_logic_vector (15 downto 0));
31     end component;
32
33     component FunctionalUnit is
34         Port ( A : in std_logic_vector (15 downto 0);
35             B : in std_logic_vector (15 downto 0);
36             FS : in std_logic_vector (3 downto 0);
37             D : out std_logic_vector (15 downto 0);
38             FL : out std_logic_vector (3 downto 0));
39     end component;
40
41     component DataMemory is
42         Port ( Address : in std_logic_vector (15 downto 0);
43             Data : in std_logic_vector (15 downto 0);
44             WR : in std_logic;
45             CLK : in std_logic;
46             DataOut : out std_logic_vector (15 downto 0));
47     end component;
48
49     signal A, B, AK, BK, DM, DF, DI : std_logic_vector (15 downto 0);
50
51     begin
52         RF1 : RegisterFile port map (CLK => CLK, DATA=> DI, WR=>WR, DA=>DA, AA=>AA, BA=>BA, A=>A, B=>B);
53         AK <= A when MA='0' else
54             KNS when MA='1' else (others => 'X');
55         BK <= B when MB='0' else
56             KNS when MB='1' else (others => 'X');
57         FU1 : FunctionalUnit port map (A=>AK, B=>BK, FS=>FS, D=>DF, FL=>FL);
58         DM1 : DataMemory port map (Address=>BK, Data=>AK, WR=>MW, CLK=>CLK, DataOut=>DM);
59         DI <= DF when MD='0' else
60             DM when MD='1' else (others => 'X');
61         D <= DI;
62     end structural;
```





VHDL – Lab1

DATAPATH

REGISTER

FUNCTIONALUNIT

DATAMEMORY

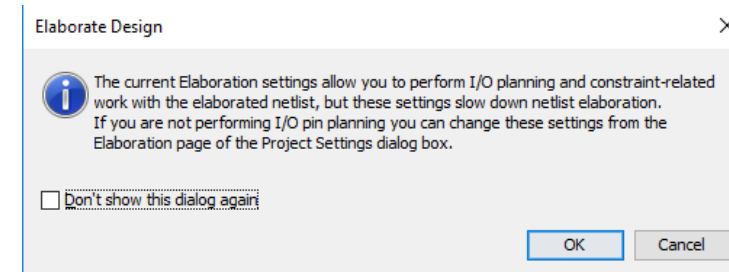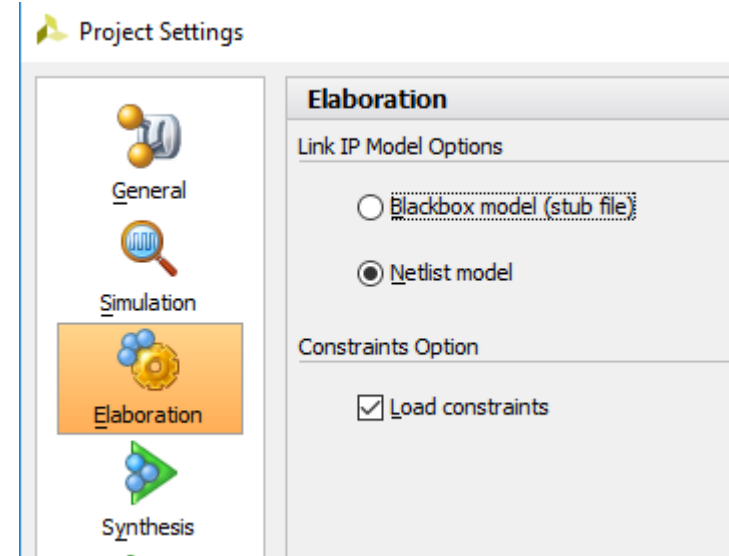 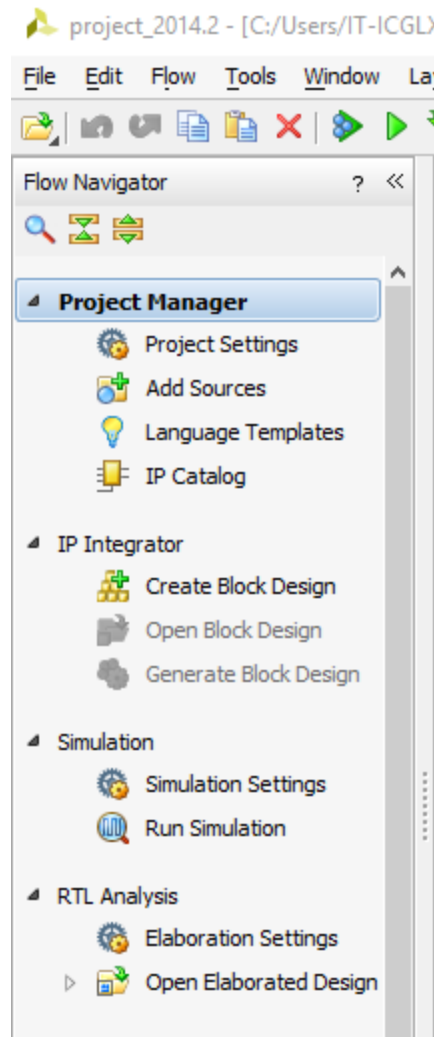



VHDL – Lab1

DATAPATH

REGISTER

FUNCTIONALUNIT

DATAMEMORY

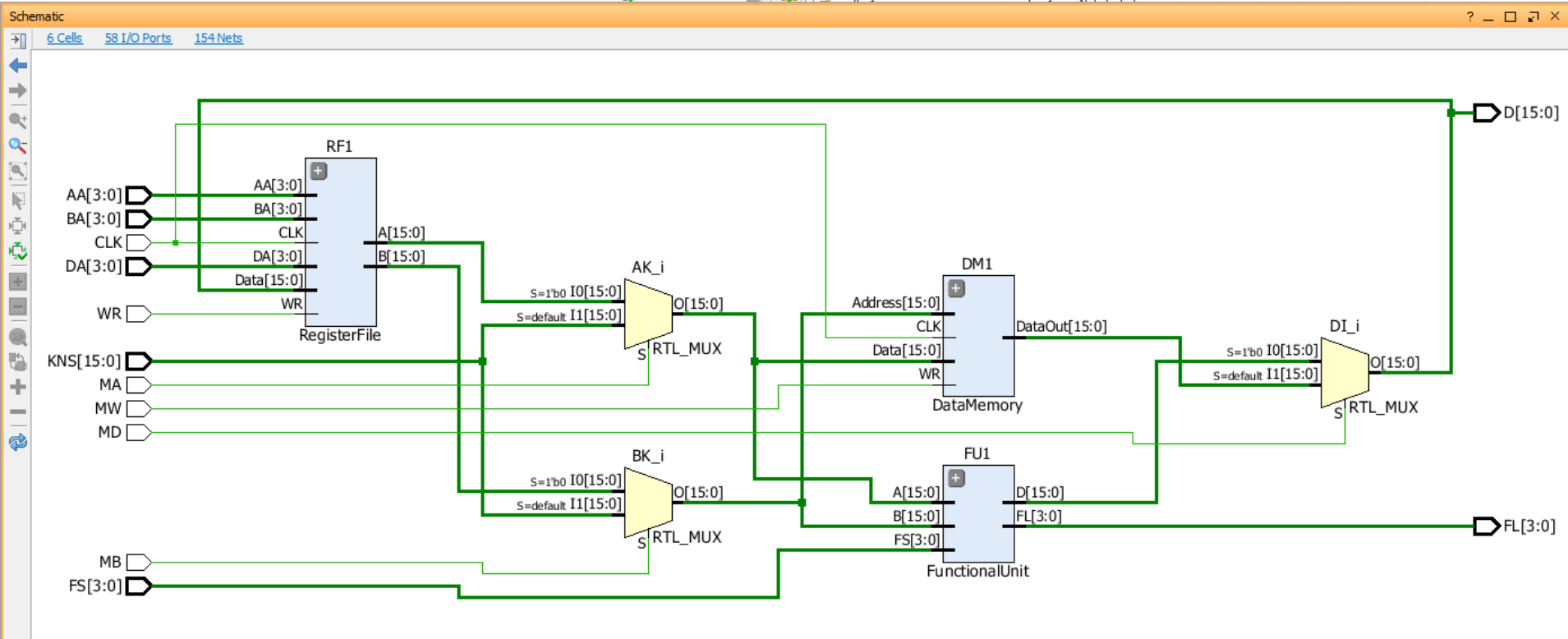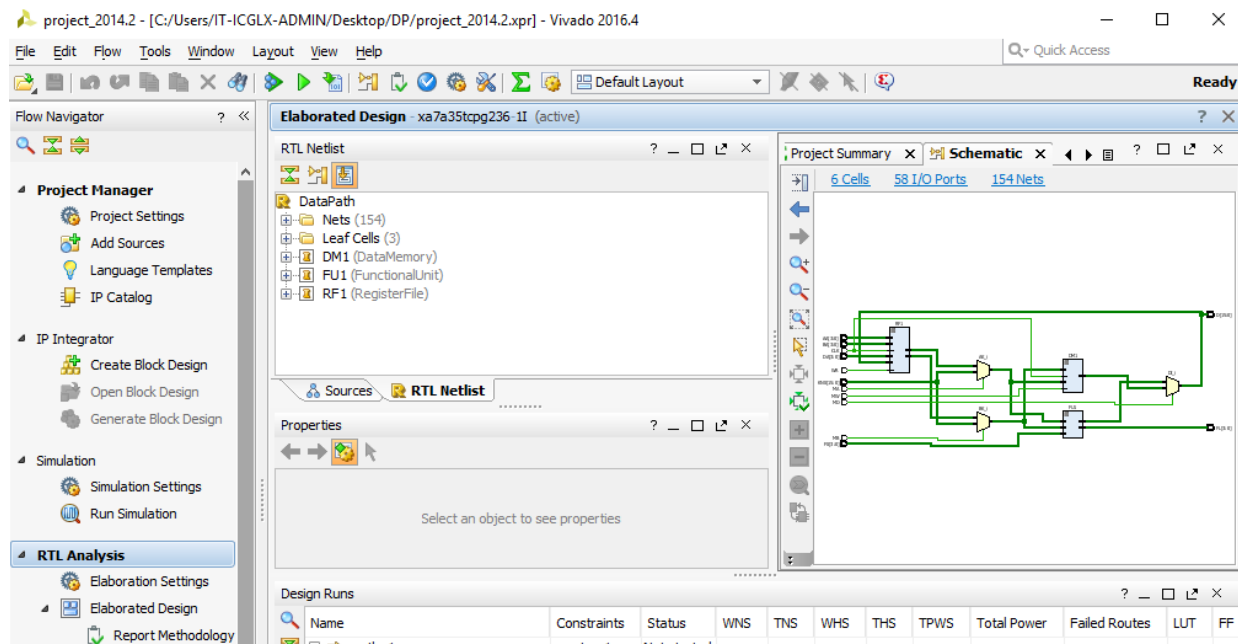

VHDL – L

DATAPATH

REGISTERFILE


REGISTER16

DECODER

MUX16TO1

RegisterFile.vhd
C:/Users/IT-ICGLX-ADMIN/Desktop/DP/project_2014.2.srscs/sources_1/imports/sources_1/new/RegisterFile.vhd

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3
4 entity RegisterFile is
5     Port ( CLK : in std_logic;
6           Data : in std_logic_vector (15 downto 0);
7           WR : in std_logic;
8           DA : in std_logic_vector (3 downto 0);
9           AA : in std_logic_vector (3 downto 0);
10          BA : in std_logic_vector (3 downto 0);
11          A : out std_logic_vector (15 downto 0);
12          B : out std_logic_vector (15 downto 0));
13 end RegisterFile;
14
15 architecture structural of RegisterFile is
16     component Register16 is
17         port( D: in std_logic_vector(15 downto 0);
18              Load: in std_logic;
19              CLK: in std_logic;
20              Q: out std_logic_vector(15 downto 0):=(others => '0')
21              );
22     end component;
23
24     component mux16to1_16 is
25         Port ( S : in std_logic_vector (3 downto 0);
26              I0 : in std_logic_vector (15 downto 0);
27              I1 : in std_logic_vector (15 downto 0);
28              I2 : in std_logic_vector (15 downto 0);
29              I3 : in std_logic_vector (15 downto 0);
30              I4 : in std_logic_vector (15 downto 0);
31              I5 : in std_logic_vector (15 downto 0);
32              I6 : in std_logic_vector (15 downto 0);
33              I7 : in std_logic_vector (15 downto 0);
34              I8 : in std_logic_vector (15 downto 0);
35              I9 : in std_logic_vector (15 downto 0);
36              I10 : in std_logic_vector (15 downto 0);
37              I11 : in std_logic_vector (15 downto 0);
38              I12 : in std_logic_vector (15 downto 0);
39              I13 : in std_logic_vector (15 downto 0);
40              I14 : in std_logic_vector (15 downto 0);
41              I15 : in std_logic_vector (15 downto 0);
42              O : out std_logic_vector (15 downto 0));
43     end component;
44
45     component Decoder is
46         Port ( A : in std_logic_vector (3 downto 0);
47              D0 : out std_logic;
48              D1 : out std_logic;
49              D2 : out std_logic;
50              D3 : out std_logic;
51              D4 : out std_logic;
52              D5 : out std_logic;
53              D6 : out std_logic;
54              D7 : out std_logic;
55              D8 : out std_logic;
56              D9 : out std_logic;
57              D10 : out std_logic;
58              D11 : out std_logic;
59              D12 : out std_logic;
60              D13 : out std_logic;
61              D14 : out std_logic;
62              D15 : out std_logic);
63     end component;
64
```

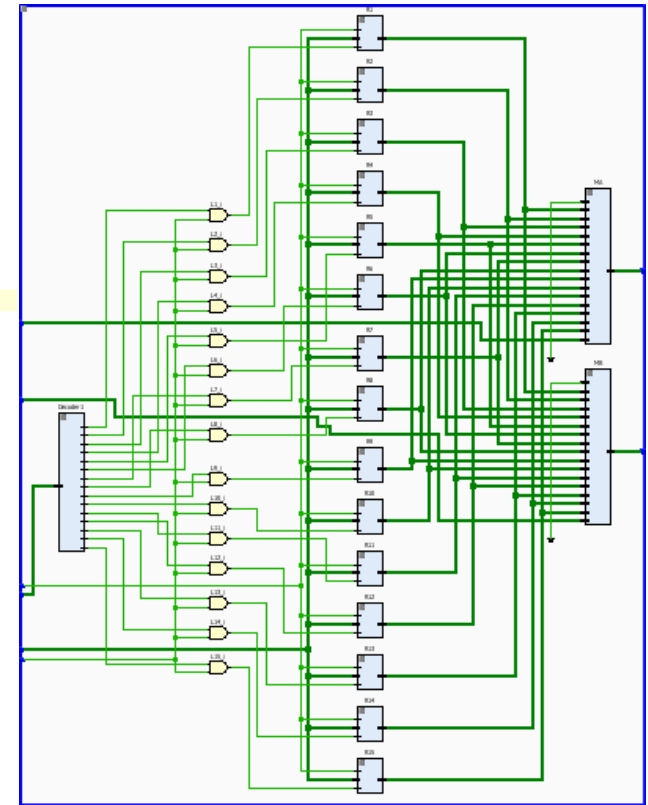

```
65 signal D0, D1, D2, D3, D4, D5, D6, D7, D8, D9, D10, D11, D12, D13, D14, D15: std_logic;
66 signal L0, L1, L2, L3, L4, L5, L6, L7, L8, L9, L10, L11, L12, L13, L14, L15: std_logic;
67 signal Q0, Q1, Q2, Q3, Q4, Q5, Q6, Q7, Q8, Q9, Q10, Q11, Q12, Q13, Q14, Q15: std_logic_vector (15 downto 0);
68
69 begin
70     Decoder1: Decoder port map (A => DA, D0=>D0, D1=>D1, D2=>D2, D3=>D3, D4=>D4, D5=>D5, D6=>D6, D7=>D7, D8=>D8,
71                                L1 <= D1 and WR; L2 <= D2 and WR; L3 <= D3 and WR; L4 <= D4 and WR; L5 <= D5 and WR; L6 <= D6 and WR; L7
72                                Q0 <= (others => '0');
73     R1: Register16 port map (D => Data, Load => L1, CLK => CLK, Q=> Q1);
74     R2: Register16 port map (D => Data, Load => L2, CLK => CLK, Q=> Q2);
75     R3: Register16 port map (D => Data, Load => L3, CLK => CLK, Q=> Q3);
76     R4: Register16 port map (D => Data, Load => L4, CLK => CLK, Q=> Q4);
77     R5: Register16 port map (D => Data, Load => L5, CLK => CLK, Q=> Q5);
78     R6: Register16 port map (D => Data, Load => L6, CLK => CLK, Q=> Q6);
79     R7: Register16 port map (D => Data, Load => L7, CLK => CLK, Q=> Q7);
80     R8: Register16 port map (D => Data, Load => L8, CLK => CLK, Q=> Q8);
81     R9: Register16 port map (D => Data, Load => L9, CLK => CLK, Q=> Q9);
82     R10: Register16 port map (D => Data, Load => L10, CLK => CLK, Q=> Q10);
83     R11: Register16 port map (D => Data, Load => L11, CLK => CLK, Q=> Q11);
84     R12: Register16 port map (D => Data, Load => L12, CLK => CLK, Q=> Q12);
85     R13: Register16 port map (D => Data, Load => L13, CLK => CLK, Q=> Q13);
86     R14: Register16 port map (D => Data, Load => L14, CLK => CLK, Q=> Q14);
87     R15: Register16 port map (D => Data, Load => L15, CLK => CLK, Q=> Q15);
88     MA: mux16to1_16 port map (S => AA, I0 => Q0, I1 => Q1, I2 => Q2, I3 => Q3, I4 => Q4, I5 => Q5, I6 => Q6,
89                               MB: mux16to1_16 port map (S => BA, I0 => Q0, I1 => Q1, I2 => Q2, I3 => Q3, I4 => Q4, I5 => Q5, I6 => Q6,
90                               end structural;
```



DEEC

DEPARTAMENTO DE ENGENHARIA
ELETROTÉCNICA E DE COMPUTADORES

TÉCNICO LISBOA

VHDL – Lab1

DATAPATH


REGISTERFILE

REGISTER16

DECODER

MUX16TO1

```
Register16.vhd
C:/Users/IT-ICGLX-ADMIN/Desktop/DP/project_2014.2.srscs/sources_1/imports/sources_1/imports/files/Register16.vhd
1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity Register16 is
5      port(  D: in std_logic_vector(15 downto 0);
6            Load: in std_logic;
7            CLK: in std_logic;
8            Q: out std_logic_vector(15 downto 0):=(others => '0')
9        );
10 end Register16;
11
12 architecture structural of Register16 is
13 begin
14     Q <= D when CLK'event and CLK='1' and Load='1';
15 end structural;
16
```

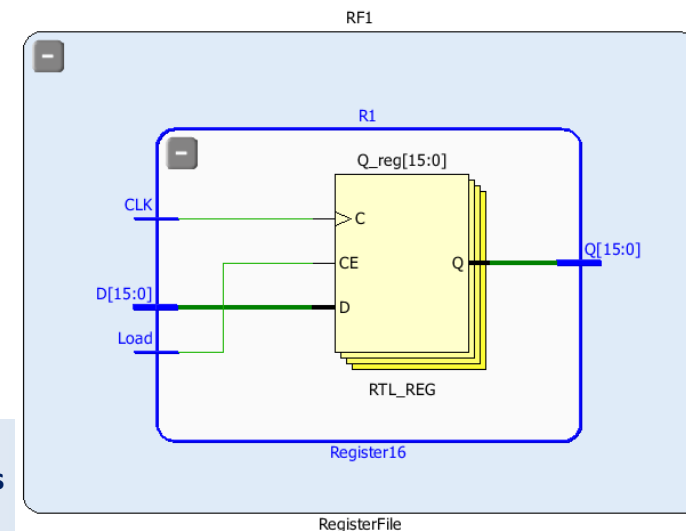

VHDL – Lab1


DATAPATH

REGISTERFILE

REGISTER16

DECODER


MUX16TO1

 

Decoder.vhd

C:/Users/IT-ICGLX-ADMIN/Desktop/DP/project_2014.2.srcs/sources_1/imports/sources_1/new/Decoder.vhd

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3
4 entity Decoder is
5     Port ( A : in STD_LOGIC_VECTOR (3 downto 0);
6           D0 : out STD_LOGIC;
7           D1 : out STD_LOGIC;
8           D2 : out STD_LOGIC;
9           D3 : out STD_LOGIC;
10          D4 : out STD_LOGIC;
11          D5 : out STD_LOGIC;
12          D6 : out STD_LOGIC;
13          D7 : out STD_LOGIC;
14          D8 : out STD_LOGIC;
15          D9 : out STD_LOGIC;
16          D10 : out STD_LOGIC;
17          D11 : out STD_LOGIC;
18          D12 : out STD_LOGIC;
19          D13 : out STD_LOGIC;
20          D14 : out STD_LOGIC;
21          D15 : out STD_LOGIC);
22 end Decoder;
23
24 architecture Behavioral of Decoder is
25 begin
26     D0 <= not A(3) and not A(2) and not A(1) and not A(0);
27     D1 <= not A(3) and not A(2) and not A(1) and A(0);
28     D2 <= not A(3) and not A(2) and A(1) and not A(0);
29     D3 <= not A(3) and not A(2) and A(1) and A(0);
30     D4 <= not A(3) and A(2) and not A(1) and not A(0);
31     D5 <= not A(3) and A(2) and not A(1) and A(0);
32     D6 <= not A(3) and A(2) and A(1) and not A(0);
33     D7 <= not A(3) and A(2) and A(1) and A(0);
34     D8 <= A(3) and not A(2) and not A(1) and not A(0);
35     D9 <= A(3) and not A(2) and not A(1) and A(0);
36     D10 <= A(3) and not A(2) and A(1) and not A(0);
37     D11 <= A(3) and not A(2) and A(1) and A(0);
38     D12 <= A(3) and A(2) and not A(1) and not A(0);
39     D13 <= A(3) and A(2) and not A(1) and A(0);
40     D14 <= A(3) and A(2) and A(1) and not A(0);
41     D15 <= A(3) and A(2) and A(1) and A(0);
42 end Behavioral;
43
```

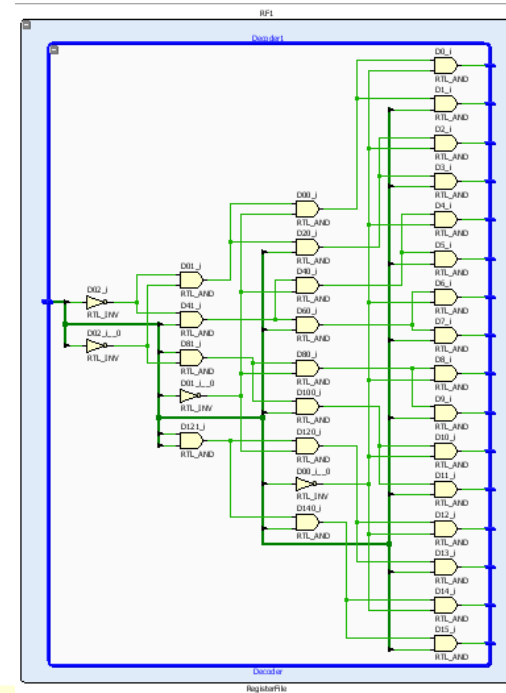

VHDL – Lab1



DATAPATH

REGISTERFILE

REGISTER16

DECODER

MUX16TO1 (A)

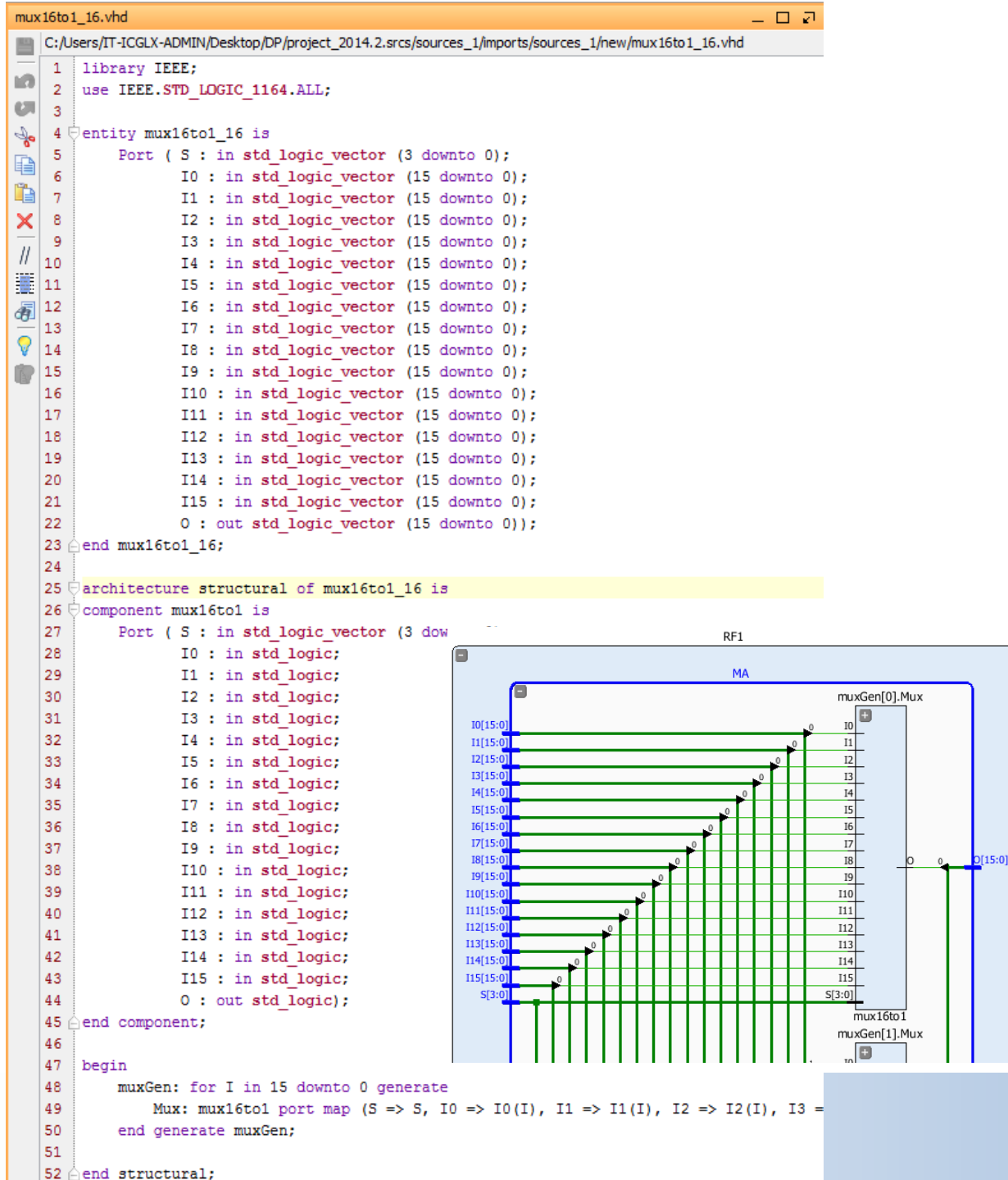 

VHDL – Lab1

DATAPATH

REGISTERFILE

REGISTER16

DECODER

MUX16TO1 (B)

```
mux16to1.vhd
C:/Users/IT-ICGLX-ADMIN/Desktop/DP/project_2014.2.srscs/sources_1/imports/sources_1/new/mux16to1.vhd

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity mux16to1 is
5      Port ( S : in std_logic_vector (3 downto 0);
6            I0 : in std_logic;
7            I1 : in std_logic;
8            I2 : in std_logic;
9            I3 : in std_logic;
10           I4 : in std_logic;
11           I5 : in std_logic;
12           I6 : in std_logic;
13           I7 : in std_logic;
14           I8 : in std_logic;
15           I9 : in std_logic;
16           I10 : in std_logic;
17           I11 : in std_logic;
18           I12 : in std_logic;
19           I13 : in std_logic;
20           I14 : in std_logic;
21           I15 : in std_logic;
22           O : out std_logic);
23 end mux16to1;
24
25 architecture structural of mux16to1 is
26 begin
27     O <= (I0 and not S(3) and not S(2) and not S(1) and not S(0)) or
28          (I1 and not S(3) and not S(2) and not S(1) and S(0)) or
29          (I2 and not S(3) and not S(2) and S(1) and not S(0)) or
30          (I3 and not S(3) and not S(2) and S(1) and S(0)) or
31          (I4 and not S(3) and S(2) and not S(1) and not S(0)) or
32          (I5 and not S(3) and S(2) and not S(1) and S(0)) or
33          (I6 and not S(3) and S(2) and S(1) and not S(0)) or
34          (I7 and not S(3) and S(2) and S(1) and S(0)) or
35          (I8 and S(3) and not S(2) and not S(1) and not S(0)) or
36          (I9 and S(3) and not S(2) and not S(1) and S(0)) or
37          (I10 and S(3) and not S(2) and S(1) and not S(0)) or
38          (I11 and S(3) and not S(2) and S(1) and S(0)) or
39          (I12 and S(3) and S(2) and not S(1) and not S(0)) or
40          (I13 and S(3) and S(2) and not S(1) and S(0)) or
41          (I14 and S(3) and S(2) and S(1) and not S(0)) or
42          (I15 and S(3) and S(2) and S(1) and S(0));
43
44 end structural;
```



DEEC

DEPARTAMENTO DE ENGENHARIA
ELETROTÉCNICA E DE COMPUTADORES

TÉCNICO LISBOA

VHDL

DATAPATH

FUNCTION

FunctionalUnit.vhd

C:/Users/IT-ICGLX-ADMIN/Desktop/DP/project_2014.2.srsc/sources_1/imports/sources_1/new/FunctionalUnit.vhd

```


1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity FunctionalUnit is
5      Port ( A : in std_logic_vector (15 downto 0);
6            B : in std_logic_vector (15 downto 0);
7            FS : in std_logic_vector (3 downto 0);
8            D : out std_logic_vector (15 downto 0);
9            FL : out std_logic_vector (3 downto 0));
10 end FunctionalUnit;
11
12 architecture structural of FunctionalUnit is
13     component ArithmeticUnit is
14         Port ( A : in std_logic_vector (15 downto 0);
15               B : in std_logic_vector (15 downto 0);
16               FS : in std_logic_vector (1 downto 0);
17               D : out std_logic_vector (15 downto 0);
18               CO : out std_logic;
19               OV : out std_logic);
20     end component;
21
22     component LogicUnit is
23         Port ( A : in std_logic_vector (15 downto 0);
24               B : in std_logic_vector (15 downto 0);
25               FS : in std_logic_vector (2 downto 0);
26               D : out std_logic_vector (15 downto 0);
27               CO : out std_logic;
28               OV : out std_logic);
29     end component;
30
31     component Shifter is
32         Port ( B : in std_logic_vector (15 downto 0);
33               FS : in std_logic_vector (2 downto 0);
34               D : out std_logic_vector (15 downto 0);
35               CO : out std_logic;
36               OV : out std_logic);
37     end component;
38
39     component Zero is
40         port( Data : in std_logic_vector (15 downto 0));
41     end component;
42
43     component Buf is
44         port( I : in std_logic; D : out std_logic);
45     end component;
46
47     signal DI : std_logic_vector (15 downto 0);
48     signal DA : std_logic_vector (15 downto 0);
49     signal DL : std_logic_vector (15 downto 0);
50     signal DS : std_logic_vector (15 downto 0);
51     signal COA, OVA, COS, OVS : std_logic;
52     signal Z, N, C, O : std_logic;

```

```

51
52 begin
53     AU1 : ArithmeticUnit port map (A => A, B=>B, FS=> FS(1 downto 0), D=>DA, CO=>CO);
54     LU1 : LogicUnit port map (A => A, B=>B, FS=> FS(2 downto 0), D=>DL);
55     SH1 : Shifter port map (B=>B, FS=>FS(2 downto 0), D=>DS, CO=>COS, OV=>OVS);
56
57     with FS(3 downto 1) select
58     DI <=  DA when "000" | "001",
59            DL when "010" | "011" | "100",
60            DS when "101" | "110" | "111",
61            (others => 'X') when others;
62
63     -- zero
64     Zero1: Zero port map (Data=>DI, D=>Z);
65
66     -- negative
67     Buf1: Buf port map (I=> DI(15), D=> N);
68
69     -- carry
70     with FS(3 downto 1) select
71     C <=  COA when "000" | "001",
72            '-' when "010" | "011" | "100",
73            COS when "101" | "110" | "111",
74            'X' when others;
75
76     -- overflow
77     with FS(3 downto 1) select
78     O <=  OVA when "000" | "001",
79            '-' when "010" | "011" | "100",
80            OVS when "101" | "110" | "111",
81            'X' when others;
82
83     D <= DI;
84     FL <= Z & N & C & O;
85 end structural;

```

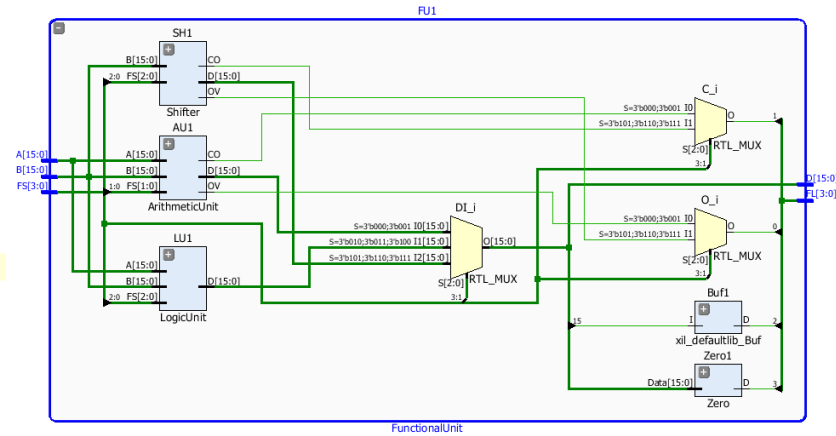

VHDL – Lab

DATAPATH

FUNCTIONALUNIT

ARITHMETICUNIT

```
ArithmeticUnit.vhd
C:/Users/IT-ICGLX-ADMIN/Desktop/DP/project_2014.2.srcs/sources_1/imports/sources_1/new/ArithmeticUnit.vhd

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity ArithmeticUnit is
5      Port ( A : in std_logic_vector (15 downto 0);
6            B : in std_logic_vector (15 downto 0);
7            FS : in std_logic_vector (1 downto 0);
8            D : out std_logic_vector (15 downto 0);
9            CO : out std_logic;
10           OV : out std_logic);
11 end ArithmeticUnit;
12
13 architecture structural of ArithmeticUnit is
14     component ArithmeticUnitI is
15         Port ( Ai : in std_logic;
16               Bi : in std_logic;
17               FS : in std_logic_vector(1 downto 0);
18               CI : in std_logic;
19               Di : out std_logic;
20               CO : out std_logic);
21     end component;
22     signal Yn : std_logic;
23     signal Z : std_logic_vector (15 downto 0);
24     signal C : std_logic_vector (16 downto 0);
25
26     begin
27         C(0) <= FS(0);
28         aritGen: for I in 15 downto 0 generate
29             AUi: ArithmeticUnitI port map (Ai=>A(I), Bi=>B(I), FS=>FS, CI=>C(I), Di=>Z(I)
30         end generate aritGen;
31         D <= Z;
32
33         -- cary
34         CO <= C(16);
35         -- overflow
36         Yn <= (B(15) and not FS(1)) or (not B(15) and FS(1));
37         OV <= (A(15) and Yn and not Z(15)) or (not A(15) and not Yn and Z(15));
38
39     end structural;
```



DEEC

DEPARTAMENTO DE ENGENHARIA
ELETROTÉCNICA E DE COMPUTADORES
TÉCNICO LISBOA

VHDL – Lab1

DATAPATH


FUNCTIONALUNIT

ARITMETICUNIT

ARUnit

```
ArithmeticUnitI.vhd
C:/Users/IT-ICGLX-ADMIN/Desktop/DP/project_2014.2.srscs/sources_1/imports/sources_1/new/ArithmeticUnitI.vhd

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity ArithmeticUnitI is
5      Port ( Ai : in std_logic;
6            Bi : in std_logic;
7            FS : in std_logic_vector(1 downto 0);
8            CI : in std_logic;
9            Di : out std_logic;
10           CO : out std_logic);
11 end ArithmeticUnitI;
12
13 architecture structural of ArithmeticUnitI is
14     component FullAdder is
15         port(X: in std_logic;
16              Y: in std_logic;
17              CI: in std_logic;
18              O: out std_logic;
19              CO: out std_logic);
20     end component;
21     signal Yi : std_logic;
22     begin
23         Yi <= (Bi and not FS(1)) or (not Bi and FS(1));
24         FA: FullAdder port map (X => Ai, Y => Yi, CI => CI, O => Di, CO => CO);
25     end structural;
26
```

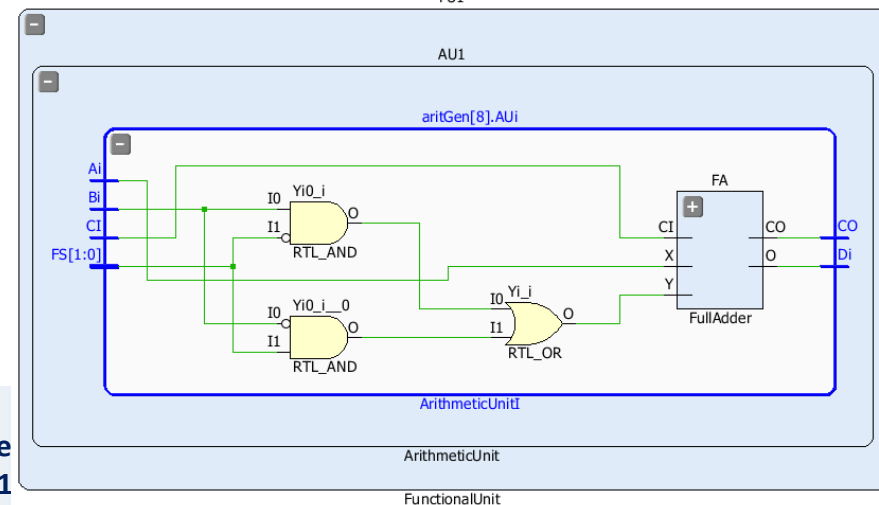

VHDL – Lab1


DATAPATH

FUNCTIONALUNIT


ARITMETICUNIT

ARUint

FULLADDER

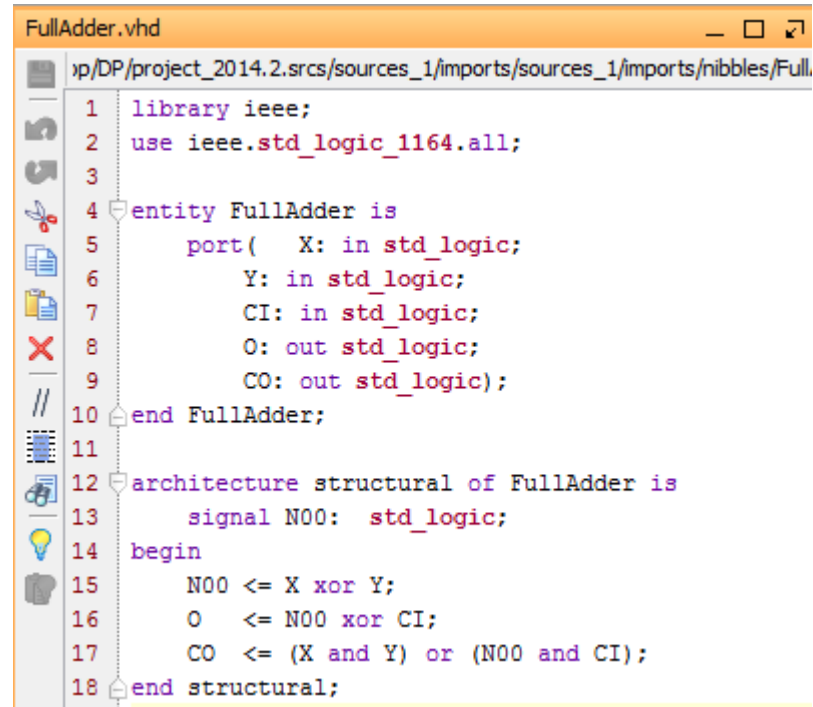

```
FullAdder.vhd
xp/DP/project_2014.2.srscs/sources_1/imports/sources_1/imports/nibbles/Full.
1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity FullAdder is
5      port(    X: in std_logic;
6              Y: in std_logic;
7              CI: in std_logic;
8              O: out std_logic;
9              CO: out std_logic);
10 end FullAdder;
11
12 architecture structural of FullAdder is
13     signal N00: std_logic;
14 begin
15     N00 <= X xor Y;
16     O    <= N00 xor CI;
17     CO  <= (X and Y) or (N00 and CI);
18 end structural;
```

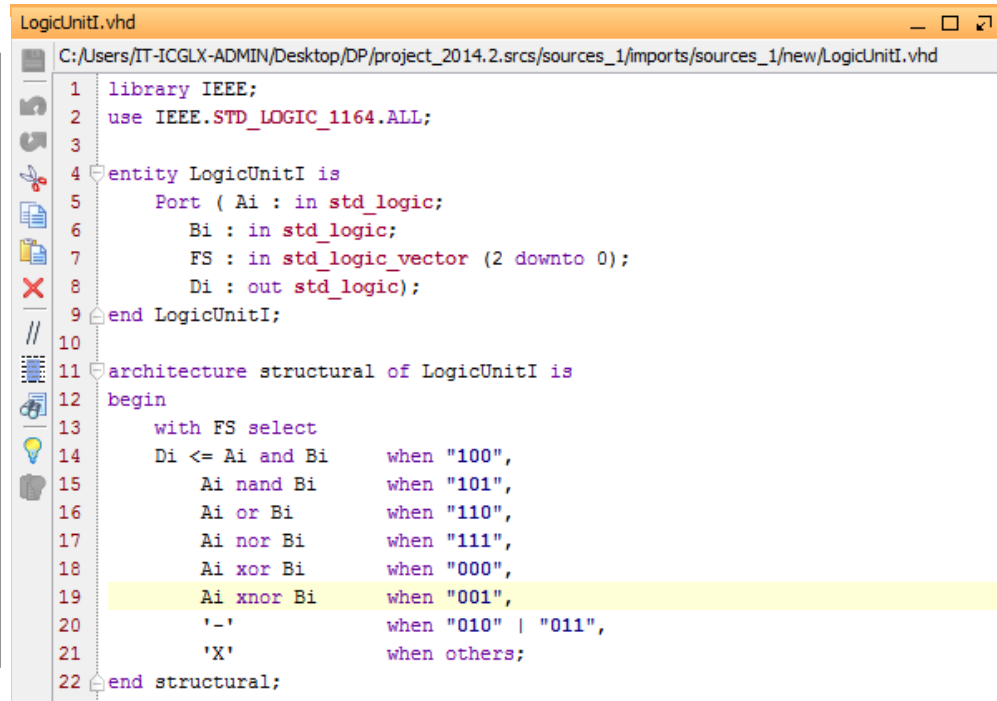
LUint

VHDL – Lab1

DATAPATH

FUNCTIONALUNIT

SHIFTER

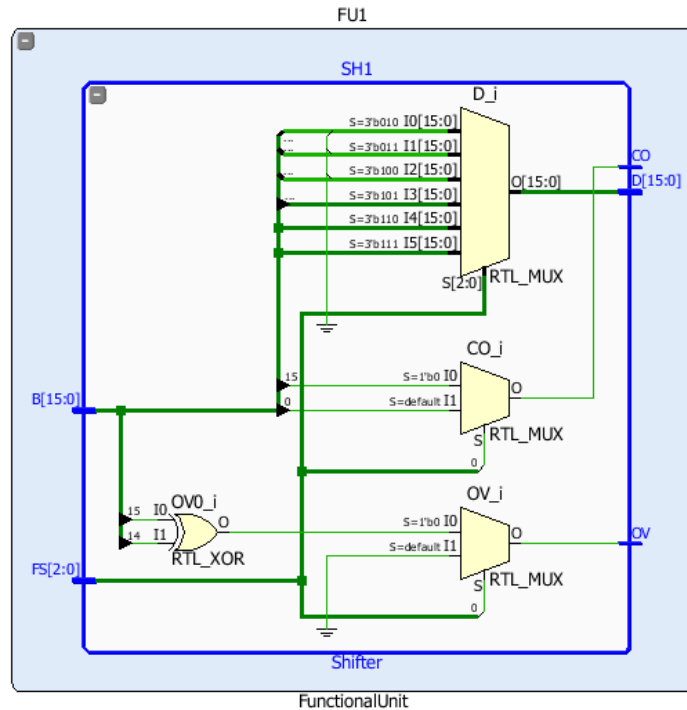

```
Shifter.vhd
C:/Users/IT-ICGLX-ADMIN/Desktop/DP/project_2014.2/srcs/sources_1/imports/source

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity Shifter is
5      Port ( B : in std_logic_vector (15 downto 0);
6            FS : in std_logic_vector (2 downto 0);
7            D : out std_logic_vector (15 downto 0);
8            CO : out std_logic;
9            OV : out std_logic);
10 end Shifter;
11
12 architecture structural of Shifter is
13 begin
14     with FS select
15         D <= (others => '-')      when "000" | "001",
16             B(14 downto 0) & '0'  when "010",
17             '0' & B(15 downto 1)  when "011",
18             B(14 downto 0) & '0'  when "100",
19             B(15) & B(15 downto 1) when "101",
20             B(14 downto 0) & B(15) when "110",
21             B(0) & B(15 downto 1)  when "111",
22             (others => 'X')       when others;
23
24     CO <= B(15) when FS(0)='0' else
25           B(0)  when FS(0)='1' else
26           'X';
27
28     OV <= B(15) xor B(14) when FS(0)='0' else
29           '0'  when FS(0)='1' else
30           'X';
31
32 end structural;
```

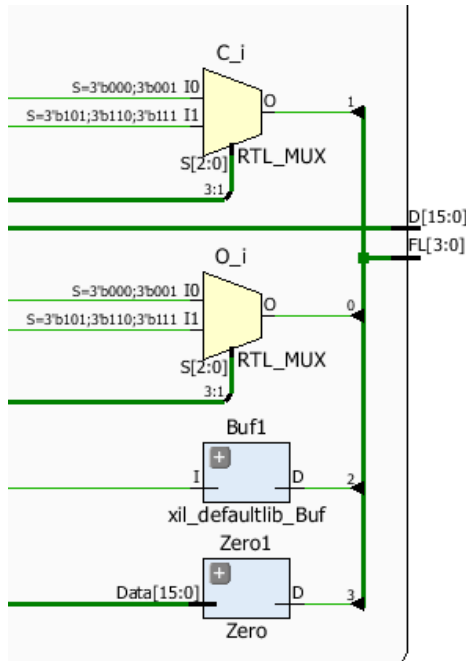

VHDL – Lab1

DATAPATH

FUNCTIONALUNIT

Zero1

Buf1




```
Zero.vhd
C:/Users/IT-ICGLX-ADMIN/Desktop/DP/project_2014.2.srscs/sources_1/imports/sources_1/new/Zero.vhd
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3
4 entity Zero is
5     port( Data : in std_logic_vector (15 downto 0);
6           D : out std_logic);
7 end Zero;
8
9 architecture Behavioral of Zero is
10 begin
11     D <= ((not Data(0) and not Data(1) and not Data(2) and not Data(3)) and
12          ((not Data(8) and not Data(9) and not Data(10) and not Data(11)) and
13          end Behavioral;
14
```

```
Buf.vhd
C:/Users/IT-ICGLX-ADMIN/Desktop/DP/project_2014.2.srscs/sources_1/im
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3
4 entity Buf is
5     port( I : in std_logic;
6           D : out std_logic);
7 end Buf;
8
9 architecture Behavioral of Buf is
10 begin
11     D <= I;
12 end Behavioral;
```

VHDL – Lab1

DATAPATH

DATAMEM

 

DataMemory.vhd


C:/Users/IT-ICGLX-ADMIN/Desktop/DP/project_2014.2.srscs/sources_1/imports/sources_1/new/DataMemory.vhd

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3 use ieee.numeric_std.all;
4
5 entity DataMemory is
6     Port ( Address : in std_logic_vector (15 downto 0);
7           Data : in std_logic_vector (15 downto 0);
8           WR : in std_logic;
9           CLK : in std_logic;
10          DataOut : out std_logic_vector (15 downto 0));
11 end DataMemory;
12
13 architecture structural of DataMemory is
14     type storage_type is array (0 to 255) of std_logic_vector(15 downto 0);
15     signal storage: storage_type := (
16         0 => x"1000",      --
17         1 => x"0001",      --
18         2 => x"0111",      --
19         3 => x"1010",      --
20         4 => x"1111",      --
21         5 => x"0100",      --
22         6 => x"1110",      --
23         7 => x"0000",      --
24         8 => x"1000",      --
25         others => x"0000");
26 begin
27     DataOut <= storage(to_integer(unsigned(Address(7 downto 0)))) when not Is_X(Address) else (others=>'X');
28     storage(to_integer(unsigned(Address(7 downto 0))))<=Data when CLK'event and CLK='1' and WR='1' and not Is_X(Address);
29 end structural;
```

Conteúdo da
Memória

VHDL – Lab1 (SIM)

DATAPATH

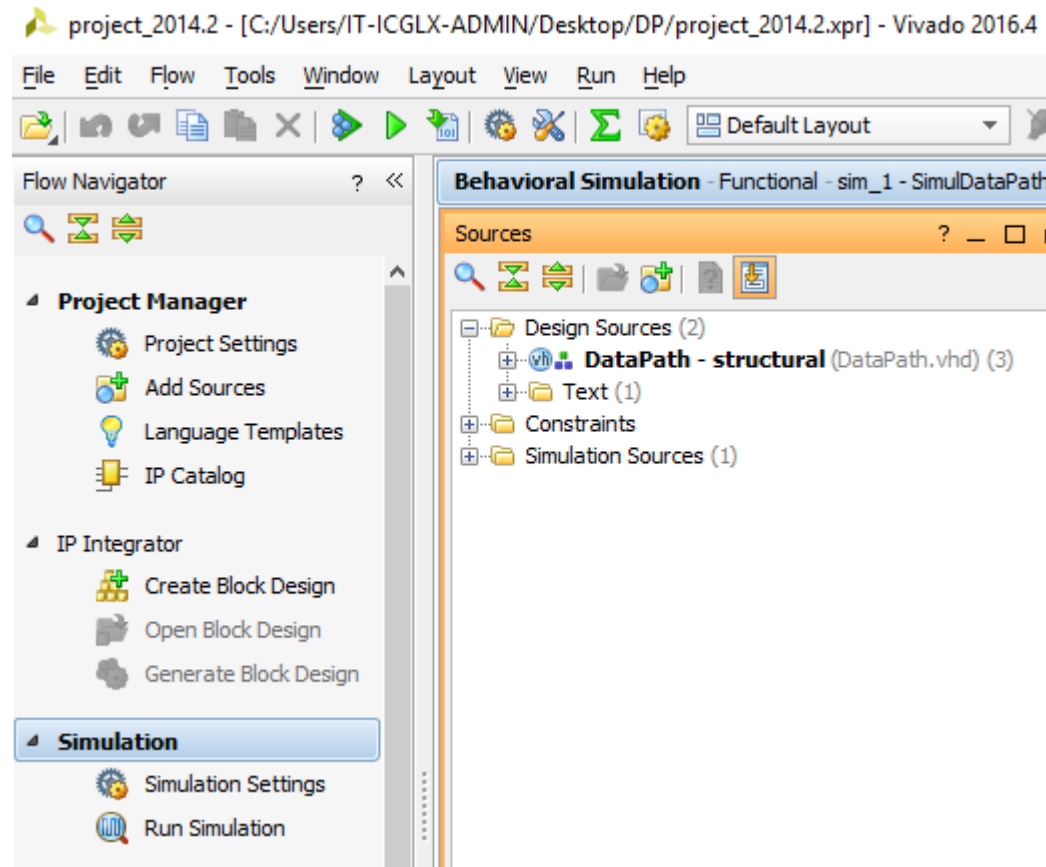

VHDL – Lab1 (SIM)

DATAPATH

```
SimulDataPath.vhd
C:/Users/IT-ICGLX-ADMIN/Desktop/DP/project_2014.2/srcs/sim_1/imports/new/SimulDataPath.vhd

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use ieee.numeric_std.all;
4
5  entity SimulDataPath is
6  end SimulDataPath;
7
8  architecture Behavioral of SimulDataPath is
9
10     function to_LVU(arg, size : natural) return std_logic_vector is
11     begin
12         return std_logic_vector(to_unsigned(arg, size));
13     end;
14
15     component DataPath is
16     Port (
17         AA : in std_logic_vector (3 downto 0);
18         BA : in std_logic_vector (3 downto 0);
19         DA : in std_logic_vector (3 downto 0);
20         WR : in std_logic;
21         MA, MB : in std_logic;
22         KNS : in std_logic_vector (15 downto 0);
23         CLK : in std_logic;
24         MW : in std_logic;
25         FS : in std_logic_vector (3 downto 0);
26         MD : in std_logic;
27         D : out std_logic_vector (15 downto 0);
28         FL : out std_logic_vector (3 downto 0);
29     end component;
30
31     signal AA : std_logic_vector (3 downto 0);
32     signal BA : std_logic_vector (3 downto 0);
33     signal DA : std_logic_vector (3 downto 0);
34     signal WR : std_logic;
35     signal MA, MB : std_logic;
36     signal KNS : std_logic_vector (15 downto 0);
37     signal clock : std_logic := '0';
38     signal MW : std_logic;
39     signal FS : std_logic_vector (3 downto 0);
40     signal MD : std_logic;
41     signal D : std_logic_vector (15 downto 0);
42     signal FL : std_logic_vector (3 downto 0);
43
44 begin
45     process
46     begin
47         wait for 50 ns;
48         clock <= not clock;
49     end process;
50
51     process
52     begin
53         wait until clock'event and clock='0';
54         -- R3 <- 2
55         AA<="1" ; BA<="1"; DA<="3"; WR<='1'; MA<='1'; MB<='0'; KNS<="0002"; MW<='0'; FS<="0"; MD<='0';
56         wait until clock'event and clock='0';
57         -- R2 <- M[2]
58         AA<="1" ; BA<="3"; DA<="2"; WR<='1'; MA<='1'; MB<='0'; KNS<="0000"; MW<='0'; FS<="0"; MD<='1';
59         wait until clock'event and clock='0';
60         -- R1 <- R2 + R3
61         AA<="2" ; BA<="3"; DA<="1"; WR<='1'; MA<='0'; MB<='0'; KNS<="0000"; MW<='0'; FS<="0"; MD<='0';
62         wait until clock'event and clock='0';
63         -- R4 <- R2 - R3
64         AA<="2" ; BA<="3"; DA<="4"; WR<='1'; MA<='0'; MB<='0'; KNS<="0000"; MW<='0'; FS<="3"; MD<='0';
65     end process;
66
67     DP0: DataPath port map (
68         AA=>AA, BA=>BA, DA=>DA, WR=>WR, MA=>MA, MB=>MB, KNS=>KNS, MW=>MW, FS=>FS, MD=>MD, D=>D, FL=>FL, CLK=>clock);
69
70 end Behavioral;
```

R3 <- 2
R2 <- M[R3]
R1 <- R2+R3
R4 <- R2-R3

VHDL – Lab1 (SIM)

DATAPATH

project_2014.2 - [C:/Users/IT-ICGLX-ADMIN/Desktop/DP/project_2014.2.xpr] - Vivado 2016.4

File Edit Flow Tools Window Layout View Run Help

Default Layout 1 us Ready

Flow Navigator

- Project Manager
 - Project Settings
 - Add Sources
 - Language Templates
 - IP Catalog
- IP Integrator
 - Create Block Design
 - Open Block Design
 - Generate Block Design
- Simulation
 - Simulation Settings
 - Run Simulation
- RTL Analysis
 - Elaboration Settings
 - Elaborated Design
 - Report Methodology
 - Report DRC

Behavioral Simulation - Functional - sim_1 - SimulDataPath

Sources

- Design Sources (2)
 - DataPath - structural (DataPath.vh)
 - RF1 - RegisterFile - structural (RegisterFile.vh)
 - FU1 - FunctionalUnit - structural (FunctionalUnit.vh)
 - DM1 - DataMemory - structural (DataMemory.vh)
- Text (1)
- Constraints
- Simulation Sources (2)
 - sim_1 (2)
 - Non-module Files (1)
 - SimulDataPath - Behavioral (SimulDataPath.vh)

Objects

Name	Value	Data Type
AA[3:0]	1	Array
BA[3:0]	3	Array
DA[3:0]	2	Array
WR	1	Logic
MA	1	Logic
MB	0	Logic
KNS[15:0]	0000	Array
clock	0	Logic
MW	0	Logic
FS[3:0]	0	Array
MD	1	Logic
D[15:0]	0000	Array
FL[3:0]	0	Array

RegisterFile.vhd x Untitled 8* x

Name	Value
AA[3:0]	1
BA[3:0]	3
DA[3:0]	2
WR	1
MA	1
MB	0
KNS[15:0]	0000
clock	0
MW	0
FS[3:0]	0
MD	1
D[15:0]	0000
FL[3:0]	0

0 ns 200 ns 400 ns 600 ns

Hierarchy Libraries Compile Order

Scope Sources

VHDL – Lab1 (SIM)

DATAPATH

Adicionar variável à simulação

project_2014.2 - [C:/Users/IT-ICGLX-ADMIN/Desktop/DP/project_2014.2.xpr] - Vivado 2016.4

The screenshot displays the Vivado IDE interface for a behavioral simulation. The 'Scopes' window on the left shows the design hierarchy with 'R2' (Register 16) selected. The 'Objects' window in the center shows the selected object 'Q[15:0]' with a value of '0000'. The 'Waveform' window on the right shows a timing diagram for various signals, including 'Q[15:0]' which is highlighted with a red circle. The waveform shows the signal's value over time, with a red circle around the 'Q[15:0]' signal name in the table.

Name	Value
AA[3:0]	1
BA[3:0]	3
DA[3:0]	2
WR	1
MA	1
MB	0
KNS...	0000
clock	0
MW	0
FS[3:0]	0
MD	1
D[15:0]	0000
FL[3:0]	0
Q[15:0]	0000

VHDL – Lab1 (SIM)

DATAPATH

